

Listen to hidden FM transmissions

# Subcarrier adaptor for FM tuners

*This simple adaptor circuit fits in your FM tuner and lets you tap into hidden FM transmissions.*

By JOHN CLARKE & LEO SIMPSON

Just recently the Department of Transport & Communications announced that it is ready to authorise subcarrier transmissions on FM broadcasts. Testing of these transmissions is going on right now and you can listen to them by building this simple adaptor circuit.

In America, subcarrier transmissions on FM broadcasts have been used for years. The Americans refer to these services as Subsidiary Communications Authorisation or SCA. It is based on a 67kHz subcarrier which is placed on the main FM carrier.

In Australia the same system is being used but it will be known as

Supplementary Monophonic Transmission (SMT) which will be generally recognised as an Ancillary Communications Service (ACS). Not a very inspiring name, is it?

Australian tests have been on single sub-carrier transmissions at 67kHz but developments in the USA provide for multiple sub-carriers, some carrying digital data and others carrying audio.

Now 67kHz sub-carrier transmissions are about to be authorised as regular services in Australia. To coincide with this, we have designed a suitable adaptor which can be hooked into most FM tuners with a


minimum of fuss. Low in cost, it uses just a few readily available integrated circuits.

Before we describe the circuit of the adaptor, let's briefly talk about FM subcarrier transmissions. They will have no effect on standard FM mono and stereo radios. Also, they will be fully compatible with all existing FM radios, whether stereo or mono. In fact, unbeknown to the great mass of FM listeners, test transmissions have been going on for some time.

But while all FM radios are presently unaffected they are able to pick up the sub-carrier transmissions and, with the addition of an adaptor such as the one we describe here, able to detect the audio signals which will generally be music.

While we were developing this adaptor circuit, the ABC in Sydney was running ACS test transmissions on 2ABC-FM. The audio modulation was the program simultaneously being broadcast by AM station 2BL. In the near future, ACS broadcasts are likely to be background music suitable for offices and factories.

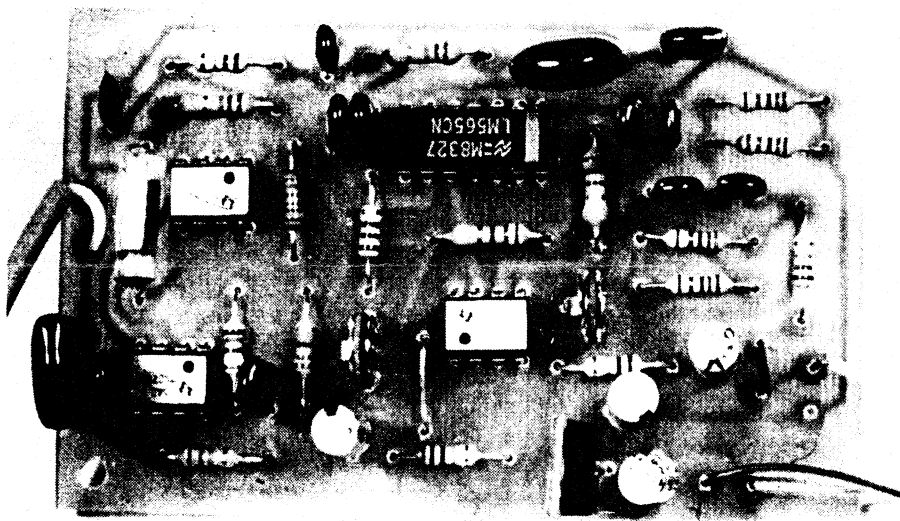SILICON CHIP'S ACS Adaptor is built on a compact printed circuit board (PCB) accommodating three low cost op amps — a phase lock loop IC, a 3-terminal regulator and a handful of resistors and capacitors.



This the ACS adaptor board, shown about 30% larger than actual size. All the parts are readily available.



signal is within the lock range of the PLL.



To minimise noise in the demodulated output, it is important to reduce the lock range of the PLL to a minimum. This is achieved by shorting pins 6 and 7 together. To a lesser extent, the lock range and therefore the noise output becomes smaller for lower input signals so we keep the input signal reasonably low without prejudicing the PLL's operation.

Following IC2 is the 18dB/octave filter employing IC3 which has a gain of one for wanted signal frequencies. This filter is followed by the final filter stage IC4 which has a gain of ten.

The adaptor is ideally powered from the tuner or receiver it is built into so we had to make its input voltage requirements non-critical. The solution is to use a 12V 3-terminal regulator which enables the circuit to be powered from any unregulated DC rail from +15 to +30 volts.

The three op amp ICs and the PLL

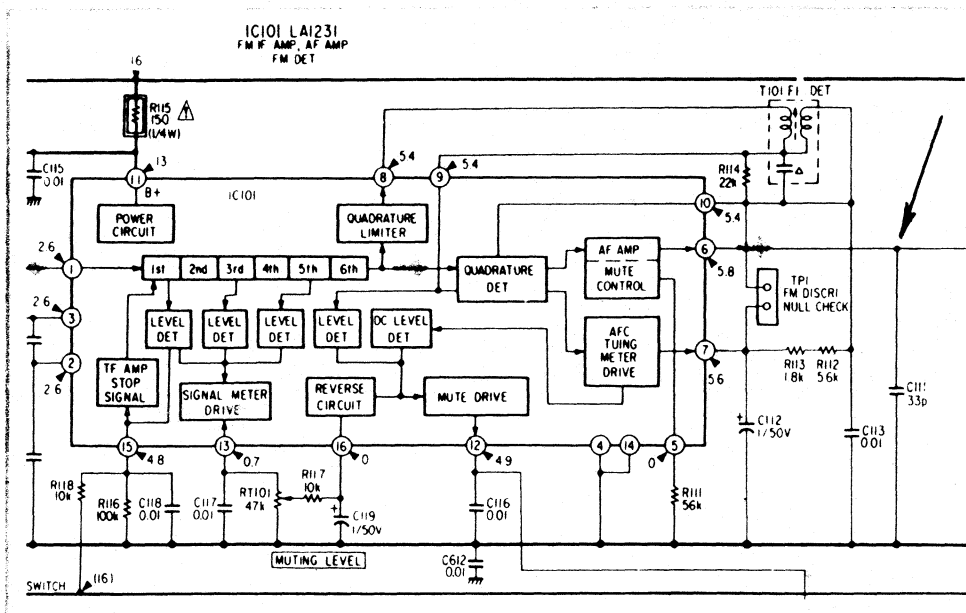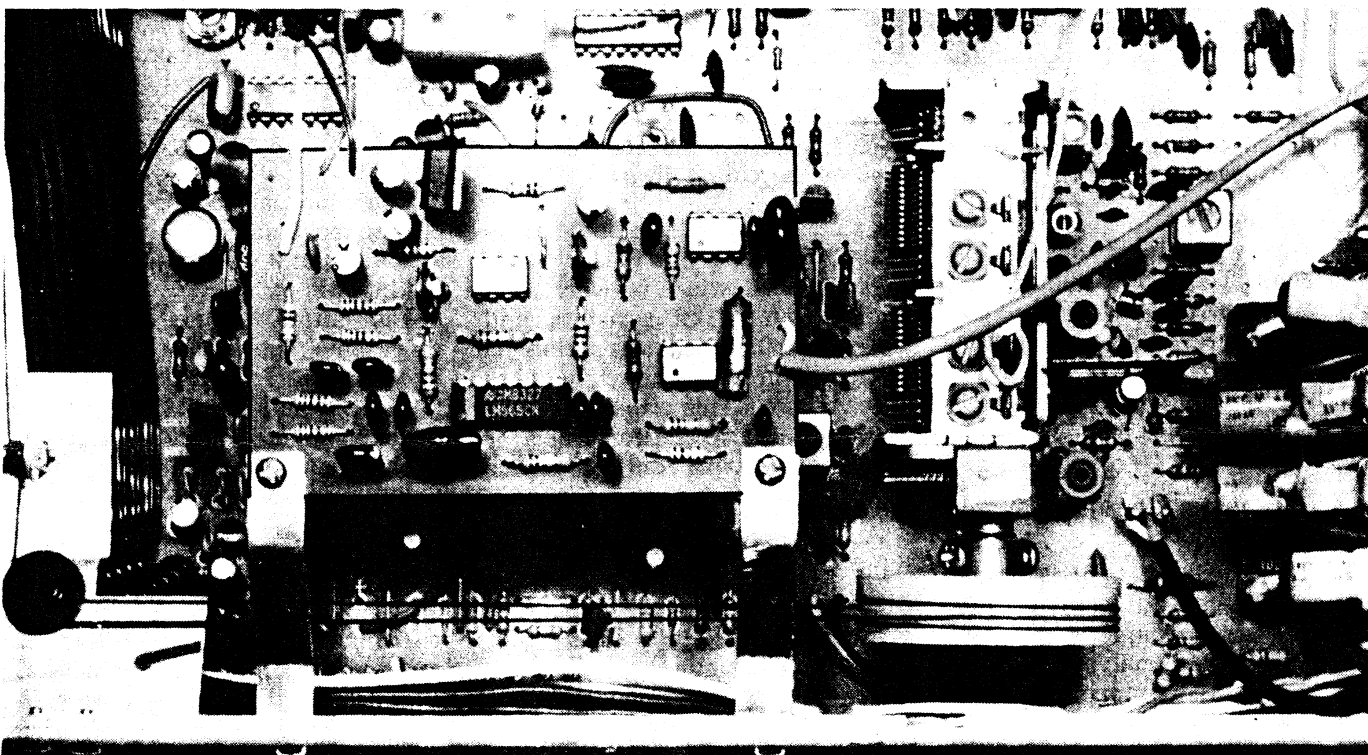This photo shows the ACS adaptor installed in an older AM/FM stereo receiver, the Harman Kardon hk570i. We used two brackets to suspend the Adaptor above the tuner board of the receiver.



are all biased to half the supply voltage by a voltage divider consisting of two 10kΩ resistors which is decoupled by a 4.7μF capacitor. The centre-point of this voltage divider is connected to pin 3 of each op amp and the PLL.

### PCB assembly

The PCB for this project measures just 57 x 89mm and is easily assembled.

No special points need to be watched when installing the parts on

the PCB except that component polarities must be correct. Note also that IC1 has a different orientation to IC2, 3 and 4.

When assembly and soldering are finished, check your work carefully and then connect a DC supply of between 15 and 30 volts. Now check the voltage at the output of the 3-terminal regulator, at pin 7 of the TL071 op amps, and at pin 10 of the PLL. In each case the reading should be close to 12V. The voltage at pin 3 of each IC should be close



setting up procedure is relatively simple.

First, make sure that VR1 is set so that its wiper is turned toward the LM565. This will provide maximum signal level. Now adjust VR2 so that there is audio signal. Find the extreme settings of VR2 where the audio signal drops out, then set VR2 halfway between the two extremes.

VR1 is used to minimise noise from the audio signal when the FM signal level is poor. Adjust the trimmer until the sound becomes distorted and then back off the adjustment until distortion is no longer audible. If you have a strong FM signal, adjustment of VR1 will have no effect on the noise level and so it should be left at its maximum resistance setting.