



### FM STEREO TRANSMITTER

**Fig.1:** the key component in the circuit is the BA1404 FM stereo transmitter IC from Rohm Corporation. This chip includes a 38kHz multiplexer plus all the necessary input amplifiers, mixers and oscillators required for FM stereo transmission.