

# When I Think Back...

by Neville Williams

## Vintage radio receiver design — 8: The evolution of table and mantel models

The majority of Australian mains powered receivers in the 1930's were 4/5-valve floor model superhets as already discussed, but the 'second set' concept generated a supplementary demand for 3/4-valve 'table' and 'mantel' models. These shared much the same basic technology, but were subject to quite different design objectives.

Before embarking upon this further dimension of receiver design, it may be appropriate to 'clear the decks' by commenting on an aspect of domestic dual-wave sets, large or small, which had to be held over from the last article. I refer to tuning systems of the day, and the frequent difficulty in locating and/or identifying individual short-wave stations.

In place of the humble 0-100 celluloid vernier dials that characterised console receivers in the early 1930's, the models that followed later in that decade were commonly fitted with comparatively large, edge-lit glass dials that offered a more striking and informative display. Blue/green sailing ships seemed to be the preferred motif, surrounded by an array of local and interstate station call signs.

As well, multiband sets carried shortwave calibrations in metres and kilocycles, plus the odd overseas transmitting centre: London, Paris, Rome, New York, etc.


Unfortunately, and despite the sometimes pretentious graphics, the shortwave calibrations indicated, at best, where overseas stations would most likely be found — and then only by careful and attentive tuning! Virtually all domestic shortwave receivers suffered from this same limitation, for which there was a compelling technical reason:

To take in the broadcast band, multiband receivers had to be fitted with a standard tuning gang of about 415pF maximum, in order to cover from around 550 to 1600kHz — a ratio of about 3:1, embracing a total bandwidth of about 1000kHz.

On a typical dial scale, a local AM broadcast band station might spread over

6mm or more, making it relatively easy to identify and to tune for the best sound.

When switched for shortwave coverage, the same tuning gang would still span a ratio of 3:1 (e.g., 13.5 - 40.5 metres), which represented a useful segment of the shortwave spectrum. But this was/is equivalent to 22 - 7.4MHz, embracing a total bandwidth of over 14,000kHz — fourteen times that of the broadcast band.

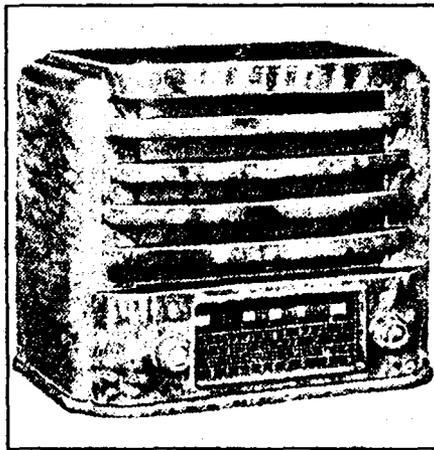

**Fig.1: A Kriesler 'compact' D/W receiver, as advertised in our November 1939 issue. In a moulded cabinet, with a choice of five colours, it retailed for around £13 (\$26).**

Since an AM shortwave station occupies only the same 20kHz-odd of bandwidth as an AM broadcast transmitter, it follows that with such a tuning range it will occupy only about one fourteenth of the dial space — even for a strong signal.

That amounts to only about one-half

millimetre, or the thickness of a pointer or calibration mark.

To make matters worse, neither the circuitry nor the mechanics of an ordinary analog (tunable) domestic receiver could/can be held to an accuracy equivalent to the width of a line on a large dial. So a shortwave station of specified frequency will rarely coincide with the dial calibration — and even if one goes searching for a particular signal, it will be less than a millimetre wide, and therefore very easy to overlook.

It helps if the dial mechanism can be made as smooth as possible and free from backlash but, at best, it is difficult to locate and identify shortwave stations relying purely on dial markings. A few models featured double-vernier drive knobs and/or supplementary 'band-spread' pointers, but they could offer only very limited assistance with what remains a fundamental limitation of ordinary tunable domestic multiband receivers.

Now to take up the main theme of this present article:

### Smaller, simpler, cheaper?

Scaled-down superhet receivers, using mostly three valves and a rectifier, were an integral part of the world radio scene for so long that, like the proverbial poor, they seemed always to have been with us. However, when I began to reflect on the matter, I realised that such was not the case. They had had a belated marketing timetable in Australia, and a design philosophy all of their own,

With hindsight, it became evident that, when mains-powered 4/5-valve superhets won acceptance in the early 1930's





cheaper to replace them when they failed, than to have them repaired.

By contrast, John said, while local demand for small receivers was rising, Australian listeners had become conditioned to conventional receivers in large cabinets — so much so that most would find it both 'amusing and interesting to hear music and speech coming from a small **box** only a few inches either way'.

*Wireless Weekly*, he said, had featured the '4/38' mantel receiver during the previous year, reducing the usual 4/5-valve complement by omitting the voltage amplifier and driving the output pentode directly from the detector. As some local manufacturers had found, the resulting gain was sufficient for day-to-day broadcast reception but **insufficient** for use on the shortwaves. This time around, *R & H* wanted to do better than that.

In a quest for higher gain, the editorial team had considered resorting to a reflexed IF/audio stage, but were deterred by the difficulties that others had encountered with the idea. (Reflexing was discussed on pages 38-39 of our June 1991 issue).


### A little 'big' set!

As it **turned out**, the *R & H* team came up with an ambitious 3/4-valve circuit, as shown in Fig.3, which provided the same **sequence** of stages as a normal 4/5-valve **superhet**! In short, it met what they saw, at the time, as a minimum requirement for any Australian family receiver — be it large or small. The circuit is interesting in its own right.

A 6K8-G served as the frequency changer, with a common feed resistor for the screen and oscillator anode — a configuration which (in the case of the 6K8) was said to counteract the effect of supply voltage variations, minimising oscillator frequency shift and the associated **risk of 'motorboating'**. **Shortwave** coverage could be provided by replacing the single coils shown in the circuit with a readily available dual-wave coil **bracket**.

From the frequency changer, the signal passed to a 6F7, an imported American double valve containing a triode and a variable-mu pentode section, independent **except** for a common cathode. With pentode characteristics very like those of a **6B7S/6G8-G**, the 6F7 could serve as a normal IF amplifier stage, with AGC control.

After 1 IF amplification, the signal passed to **two** diodes in a **European** duodiode output pentode — a valve with **about** twice the transconductance -- and therefore power gain — of the 6V6. Its intended role was for use in 3/4-valve su-

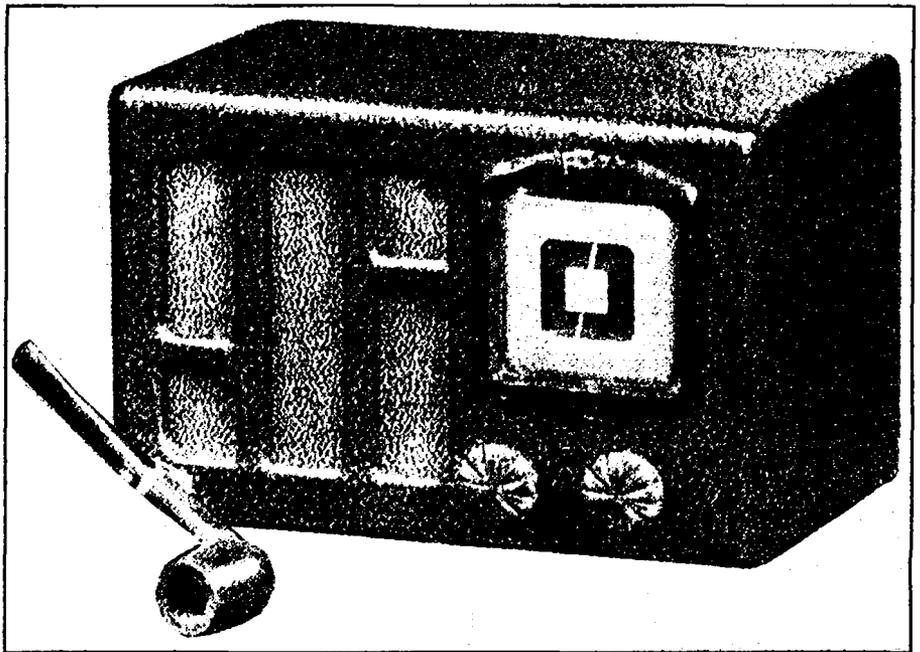

**Fig.5:** The original 'Little General; in its inexpensive leatherette covered cabinet. The one-piece escutcheon and dial scale pushed in from the front, the 'pointer' being a white line on a drive drum fixed to the shaft of the tuning gang.

perhets, operating directly from the detector output.

In the 4/39, however, the signal was passed back through the 6F7 triode section for prior amplification. With an amplification factor of 8, similar to that of the early type 27 triode, the stage gain was quite low. However, when feeding an **EBL1**, and in the absence of negative feedback, the overall audio gain would not have seemed all that different to the user from a conventional 4/5-valve superhet.

An interesting aspect of the circuit was that it used back-bias for all stages, including the AGC system. Without going into details, this allowed all cathodes to

be grounded, thereby avoiding the complications which might have arisen in providing self-bias for the multi-purpose cathodes in the 6F7 and **EBL1**. The bias levels were set to keep the current drain within the capabilities of the specified 40mA power **transformer**.

Superlatives were not spared in describing the appeal and performance of the 4/39: at 10W x 7D x 811 inches (25 x 18 x 20cm), it was 'small enough to take with you on holidays'.


Again: 'on the broadcast band there appears to be nothing that it cannot tune in'. And: 'if there is anything on the shortwave bands worth listening to, you will hear it at excellent strength'.

### 'A new star arrives'

Despite the apparent enthusiasm, less than a year had passed (April 1940) before John Moyle was waxing equally eloquent about a new midget receiver which the *R & H* staff had developed in the meantime.

It would appear that a few month's experience with 4/39 had confirmed the appeal of a receiver that could be carried at will into the kitchen, the sewing room, the workshop or the kids' bedroom for music, news, race results or whatever. But what had also become abundantly clear was that the set was rarely if ever tuned to interstate or overseas stations. For the role of a personal or 'second' set, the 4/39 had clearly been over-designed.

So the emphasis in the new receiver (Fig.4) was on portability, simplicity and

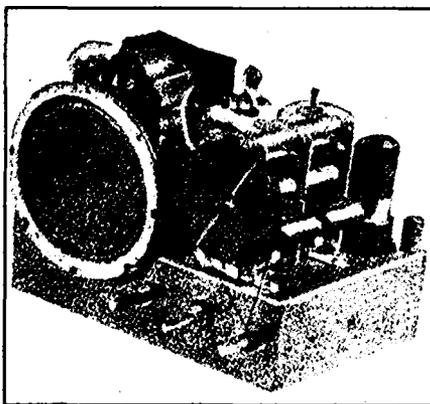

**Fig.6:** The completed chassis of the 1946 little General. It differed from the original mainly by the inclusion of one of the options, the fitting of a dual-wave bracket, accounting for the extra (central) control shaft.



of print. (In those days, office photostat copiers were still 30-odd years down the track).

I explained in the preamble that, while smaller valves and components were on the horizon, the most realistic course as at January 1946 was to retain the chassis, layout and cabinet of the original Little General, adapting the circuit and parts list to accommodate the components most likely to be accessible in this immediate postwar period.

Fig.6 shows the completed chassis, which looked essentially similar to the original version. The dial kit, probably from RCS Radio, involved a moulded drum, which attached to the gang shaft, a knob spindle with a tight-fitting rubber grommet and a length of woven drive cord with tension spring. The matching escutcheon and dial scale fitted through a cutout in the front of the leatherette covered Cabinet.

The recommended circuit (Fig.7) showed a 6J8-G as the preferred frequency changer, but other valves such as the 6K8-G, 6A8-G or 6A7, which might be on hand, were suggested as legitimate alternatives.

Following the convention of the magazine at the time, the circuit showed only a single set of coils, and in fact constructors pad the option of installing a set of broadcast coils underneath the chassis.

However, the presence of three controls confirms that the prototype carried a dual-wave bracket instead, on the basis that it involved so little extra effort and outlay that we had decided to do it that way, that time around.

An octal-based EBF2-G was

nominated as the preferred IF amplifier/detector although, again, there were other options in the way of the P-based version, or the 6G8-G or 6B7S.

My choice at the time was to revert to the use of AGC rather than manual gain control, the detector and delayed AGC circuitry being exactly as might be found in the front end of a full-size 4/5-valve superhet. Output from the detector was fed directly to a 6V6-G or 6V6-GT — valves that by then were so plentiful that alternatives were not even discussed.

In the power supply, a point of note was that a definite effort was being made to discourage the use of a traditional 385/0/385V secondary and to promote a 325/0/325V rating for small receivers, to avoid needlessly high voltages and heat dissipation.

After several years of wartime shortages and uncertainties, the article was very obviously intended to re-position the 'Little General' as an important and on-going feature in the R & H repertoire of do-it-yourself projects. To borrow John Moyle's phrase, it was a clear indication that Australians were becoming accustomed to hearing music and speech coming from a small box!

According to EA's old valve receiver master index, which Jim Rowe kindly looked up for me, the Little General popped up again in August 1947 and July 1951, with a totally new version presented by Raymond Howe in September 1952.

### 'Modern' valves

Climaxing the trend set in the previous year, the 1952 version (Fig.8) discarded

once and for all the option of using conventionally based valves and specified a new chassis to accommodate only the new all-glass miniature valves, along with proportionately smaller coils and IF transformers.

Using the same size chassis and cabinet as previously, there was room above the chassis for all the major components and also for a modern edge-lit glass dial, leaving ample space underneath for uncluttered wiring. Noteworthy also was the use of a dynamic loudspeaker with a permanent magnet rather than an electromagnetic field coil — a spin-off from wartime technology.

Despite their much reduced dimensions, the new miniature valves were well ahead of the older types in terms of gain and efficiency. The 6AE8 triode-hexode converter had about twice the conversion gain of the older types, the 6BA6 offered two to three times the transconductance of earlier IF amplifiers, while the 6BV7 was way ahead of the 6V6-G and even more sensitive than the EBL1 — once the pride and joy of the Philips/Mullard range.

With overall back-bias and delayed AGC, the 1952 circuit invites obvious comparison with those discussed earlier. But allowing for a gain advantage of around 2:1 per stage, the overall sensitivity could be expected to be well up on the earlier 3-stage versions. A further point of note is that, with the use of a relatively low-resistance choke in place of the loudspeaker field coil, HT voltage drop in the filter system was less.

In addition, the indirectly heated 6X4 miniature rectifier was much more efficient than the old 5Y3/80, offering the further advantage that it did not call for a separate 5-volt filament winding. It permitted the use of a simpler power transformer delivering much lower voltage, but with a higher current rating.

Since all of the valves shown were Australian-made, along with virtually all the other components, the Little General for 1952 had a lot in common with postwar mantel receivers offered by Australian manufacturers. Some even used leatherette-covered cabinets; but in line with overseas trends, those who could cope with the initial expense came up with a variety of moulded plastic designs.

Occasionally, much to the delight of home constructors, production over-runs of such mouldings turned up later in surplus clearance dealers, giving enthusiasts the chance to accommodate their handiwork in a decidedly 'non-handyman' cabinet.

Continued on page 83

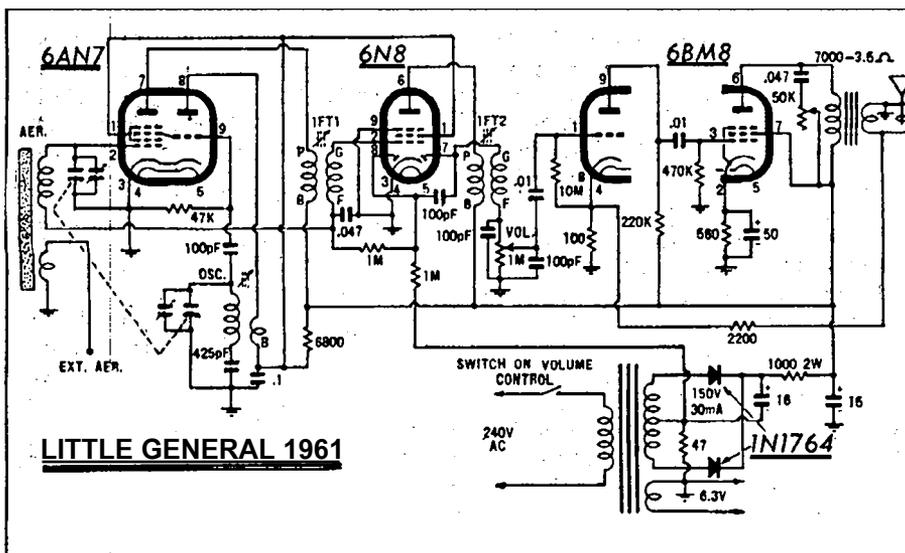


Fig.9: The last of the 'Little General' series, using what was virtually the last generation of mass produced valves. This series also featured widely in Australian monochrome television receivers, before giving place to solid-state devices:

**The final chapter**

A detailed sequence of articles in the issues June-September described the construction of the 1956 version, with the 1957 version appearing in April of that year. By that time, the situation had changed. TV broadcasting had commenced in Australia, and it was obvious that radio would no longer dominate family entertainment. ATV set would in future take the place that had been occupied for so long by the radio console. ,

For sure, radio would still have a place for casual listening — provided the set didn't take up too much room and could be moved around, as required. Quite suddenly, from being a second set, the 'Little General' type of radio had become the only one that most families needed.

The final chapter in the 'Little General' saga came in a series of articles by Alan Nutt (March-June 1961), culminating in the design shown in Fig.9. Ironically, it reverted to the basic design which had set the ball rolling in 1939: a four-stage circuit using three valves — this time Philips all-glass 9-pin miniatures, manufactured in Australia and equally popular with commercial manufacturers.

A 6AN7 triode-hexode converter was fed from a ferrite-rod loopstick, in lieu of an antenna and antenna coil. This was followed by a 6N8 duo-diode pentode, doing the job of a 6G8-G/6B7S, but much more efficiently. Last but not least, the 6BM8 provided a high-gain triode audio stage and a high-gain output pentode, expressly intended for that role.

The valve rectifier had disappeared, to be replaced by a pair of semiconductor power diodes — the first step to what was soon to follow, with all valves being replaced by solid-state devices.

In the meantime, what happened to the negative feedback, which was featured in the later 4/5-valve and larger receivers? In brief, negative feedback was/is fine if: (1) There is gain to spare; (2) The circuit is amenable to its use; and (3) The loudspeaker and baffle system is of sufficient quality to justify it. Faced with these prerequisites, most small-set designers said: 'Forget it'

Within a few years, anyway, Australian valve/mantel sets would be rendered obsolete by imported transistor portables featuring optional mains/battery operation and multiband reception — not in response to Australian demands, but because they were universal designs intended for world markets! ♦