

VINTAGE RADIO

by Roger Johnson

The Zenith Trans-Oceanic: 'Royalty of Radios'



There are collectable radios and collectable radios, but the Zenith Trans-Oceanic seems to have attracted a mystique of its own and has almost cult status.

THE TERM 'ROYALTY of Radios' is actually the title of a book on Zenith Trans-Oceanics by Bryant and Cones, which covers the complete history and how to identify a given model from the serial numbers, etc. But alas it contains no circuits.

The inspiration for this month's column actually came about when I was requested to repair a Trans-O. At that stage I had never actually seen one of these sets, let alone had any experience using one. So it was a matter of searching the internet, to see what information was available, troubleshooting tips and so on.

Having had to go through this research and then tackle the job, I thought it would be a waste not to pass on what I found. If you too have an interest in vintage radios I think you'll find it quite good reading.

Background

Punching 'transoceanic' into my search engine came up with the goods. The brief history that follows is largely taken from 'Padgett's Trans-Oceanic Page' (dot com?). So too did a reprint of the US Army Technical Manual for the military version, called the R520B!

An exact circuit for the model concerned, alignment instructions and coil assembly layout was obtained from a mail-order house in the US, whose e-mail address was found whilst browsing the net.

Trans-Oceanics were first released by Zenith in 1942 as the 'Clipper Deluxe' model 7G605 covering six bands: the AM broadcast band, and then five bandspread shortwave bands, viz. 49M, 31M, 25M, 19M and 16M. Production was suspended in April 1942 for wartime commitments.

Post war, the model 8G005 was released from 1946 to 1949, covered the same wavebands, and according to the research material, had 8 'loctal' tubes. It was this model that had the optional adapter and



Fig.1: The Zenith Trans-Oceanic L600 in all its glory. It dates from 1954.

switch for 220V AC operation.

Also released in 1946 was a budget priced G6004Y 'global' model, covering the broadcast band and the rather unusual short-wave band covering 9.5 - 12.1MHz; and also the G6001 'universal' version, a broadcast (BC) band only model where the name signified only operation from AC or DC power mains, or batteries. Sales of the 6G004Y were poor, and production did not continue.

From 1950 to the end of the valve models in 1962, there are more similarities than differences. Assiduous collectors will no doubt identify and spot all the nuances at 100 paces.

It would appear, for the sake of brevity, that the features common to all those models were: (a) the similar looking carrying case; (b) the use of the curiously called 'wave magnet', which in reality is a loop-coil antenna for the broadcast band; (c) battery and mains operation, and mains operation for 110V AC, 110V DC and 220V AC; (d) tube types 1L6, 1U4, 1U5 and 3V4 and a type 50A1 'barretter' (current regulator) tube; and (e) coverage of seven bands, namely BC, 2-4MHz and 4-8MHz general coverage/marine, and four shortwave bandspread bands for the 16, 19, 25 and 31 metre bands.

Construction & finish

Like most American gear of the era, it is bold, solid, artistic, looks-as-though-it-should-work and well put together. The carrying case is made of timber and standard models were covered in what we call 'leatherette' but Americans refer to as 'staghorn'.

There is a lift-up flap covering the dial and controls, and a hinged rear panel. Also included are comprehensive log charts. Deluxe models were covered in leather, but cost another US\$20 to buy. (Trans-O's sold for about US\$120 at the time — very pricey by contemporary Australian standards.)

Band selection is via self-cancelling push buttons. Included is a whip antenna for short waves, external antenna and earth connections, the 'wave magnet' which doubles as a direction finder, and a VERY effective series of four tone control switches referred to as the 'Radiorgan'. The single dial lamp is supplied with its own separate battery, pushbutton activated, and there seems no provision to operate the dial lamp from the external power source!

All in all, it is a most attractive unit, and whether the performance was good or otherwise, the very appearance just reeks of quality. American philosophy was that a top performer should look like a top performer. (I agree!)

Additionally, all components were treated against moisture and other climatic conditions to enable it to obtain optimum performance anywhere in the world, regardless of the prevailing climate.

Incidentally the 'wave magnet' has a special extension cable, and is detachable from its position in the case to enable it to be placed against the window of cars, planes or trains.

The circuit

The model which I was asked to repair was an L600 (chassis type 6L40) of 1954 vintage. Apparently, this model is similar to the military version. The circuit is a well designed five-tube superhet consisting of a type 1U4 tuned RF amplifier, a type 1L6 mixer/oscillator, a 1U4 as 455kHz IF amplifier, a 1U5 detector/audio amp, and a 3V4 in the output. The power supply is transformerless, consisting of a half-wave selenium rectifier with current regulation for the series-connected filament chain via the 50A1 barretter.

As mentioned the wavechange facility is via self-cancelling pushbuttons in an extremely complex switching arrangement. Each switch bank consists of two rows of up to 12 pairs of contacts, and in the actual switching, carefully designed connecting bars connect between selected groups of contacts, such that adjacent pairs are connected to each other, connected to opposite contacts, or become open circuit, and in the process connect the correct coil in circuit and in some cases, short-circuit coils that are not

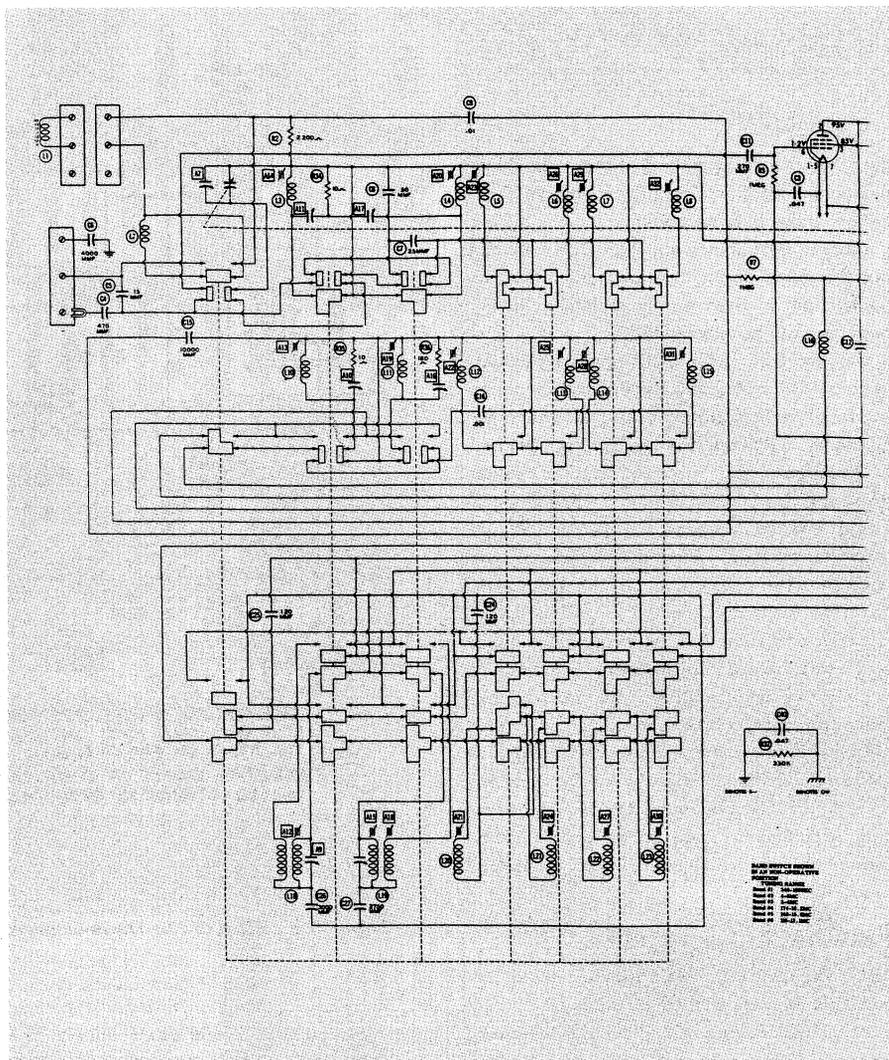


Fig.2: The complicated band switching of the L600's front end.

used. The front end is shown in Fig.2 to give an idea of the complexity.

Although complicated, the front end doesn't hold any real surprises. Moving on, though, we find a rather unorthodox IF amplifier. Instead of supplying the screen of the 1U4 via a normal dropping resistor of around 20k and bypassing it with the time-honoured 0.1uF, the designers 'decoupled' the anode circuit with a 1k resistor and a 3nF capacitor. The screen and the cold side of the IFT are supplied from this point.

In reality, the 3nF capacitor in conjunction with the 1k 'isolation resistor' provides a feedback path to the screen, to neutralise the signal grid-plate capacitance. With a carefully chosen value of capacitor (3nF), the gain of the IF amplifier can be increased considerably without causing it to self oscillate.

The tone control

The 'radiorgan' tone control is also very unorthodox, but very effective. An exploded diagram is shown in Fig.3. It depends on an inverse feedback voltage obtained from a ter-

tiary winding on the output transformer, fed back to the volume control. (Let's hope the set doesn't have any difficulties here, because a special transformer core would have to be re-wound in the event of an open-circuit primary.)

The diagram shown is taken from the military version, but is in every way similar to the 6L40 apart from part numbers. The tone control resistor-capacitor network consists of R16, R17, R32, R33, R34, R35 and capacitors C47, C48 and C49. R32/33/34/35 form a voltage divider across the tertiary winding of T3.

The function of the four switches is to alter the R-C network frequency characteristic, which results in a change to the audio response. C48 in parallel with R33 makes the network frequency dependent. When the S2B 'Bass' switch is open, as well as S2D being open, C48 in effect reduces the value of R33 at the higher frequencies. The out-of-phase higher frequencies appearing at the junction of R17/32/33 are increased, and are mixed with the high frequencies from the

