

The mouse that roared (in SSB)!

Upgrading the Tucker Tin SSB transmitter

Originally described in the February, March and April 1972 issues of "Electronics Australia," the Tucker Tin Mk 2 SSB transmitter has proved a popular project with radio amateurs. Here the author, himself a radio amateur, relates his experiences in constructing the Tucker Tin, and details several design improvements.

by PETER R. JENSEN, VK2AQJ*

After constructing the "Tucker Tin" SSB transmitter some 12 months ago, the author experienced a considerable lack of success in getting it on air.

In retrospect this difficulty was probably due more to operator inexperience than to deficiencies in the Tucker Tin. Nevertheless it was quite obvious that considering the number of stations running well over 100 watts, a rig running 4 watts was not going to make much headway despite the few 'S' points difference. It was accordingly decided that what was required was greater power output and

the achievement of this was tackled in two stages.

The first stage involved some alterations and additions to the original Tucker Tin chassis, particularly to the power amplifier. As indicated in the accompanying schematic an 807 was included as a new output tube (and a future driver for a linear amplifier) together with its own power supply. Fortunately the original chassis design for the Tucker Tin had not been followed (as photos indicate) and there was sufficient space to include the new tube, a mains transformer, bias transformer, relays etc on the existing chassis.




A vital part of this revision to the basic design was to incorporate receiver muting and aerial changeover so that full advantage could be taken of the station antenna in the receiver.

A standard PMG relay was used, powered from the unused 5V filament winding and appropriate rectifiers and capacitors. Its first function was to switch the leads from the original transmitter key jack. Additional functions were to key the cathode ground connection to the 807; to change over the antenna from receiver to transmitter and to earth the receiver input on transmit; and finally to provide receiver muting.

In passing it should be noted that the 5MHz trap included in the tank circuit of the original Tucker Tin was dispensed with—originally the new stage it proved to be unnecessary.


Another essential part of the first stage of the modification program was then undertaken. The author discovered that in order to fully modulate the signal, using the Japanese manufactured dynamic microphone available, an addi-

*7 Union St, Mosman, NSW 2088.

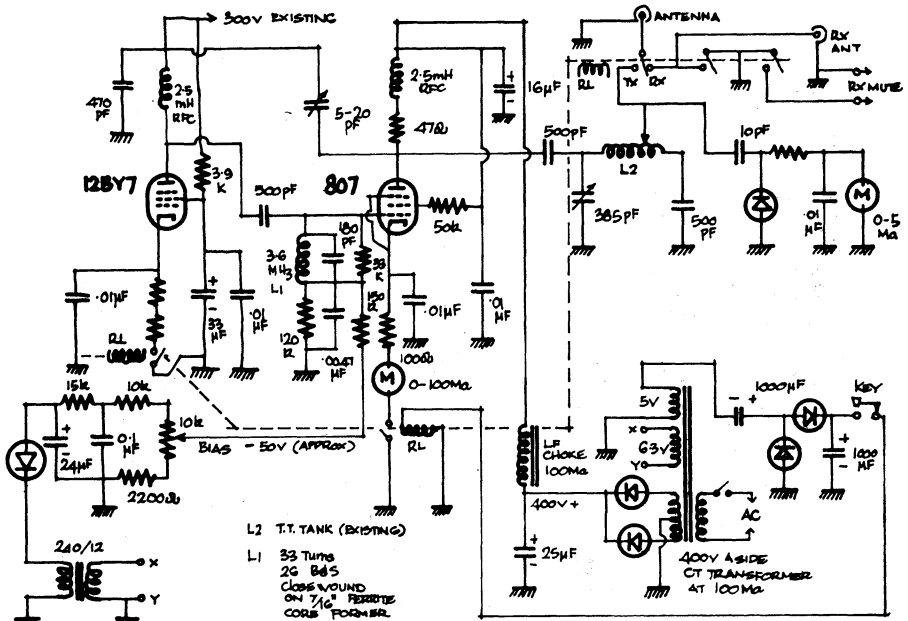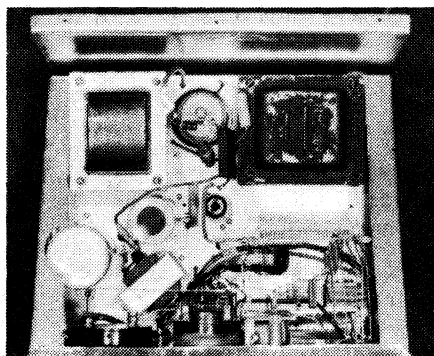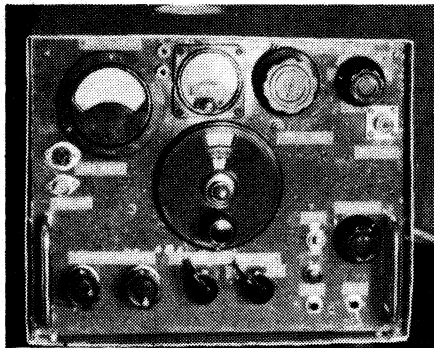

The revised power amplifier incorporates an additional stage (807) and has provision for aerial changeover and receiver muting. At left are two views of the modified Tucker Tin SSB transmitter as constructed by the author.

Upgrading the Tucker Tin Mk II

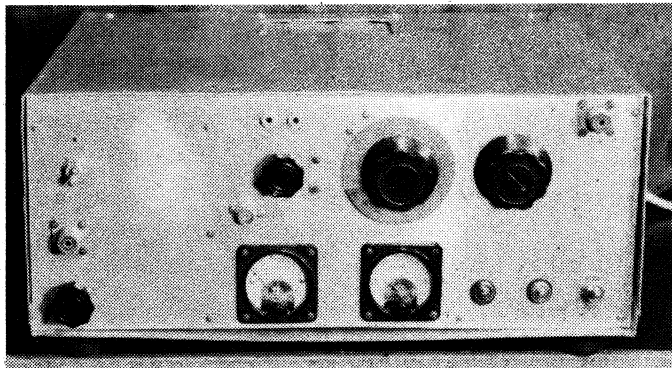


A view of the completed linear amplifier. The meters shown monitor RF output and output tube cathode current.

filament transformer for the 813 is available from Ferguson Transformers and supplies 5 amps at 10 volts.

Normal RF techniques were employed and the device worked first time. This was probably because the author was very careful in wiring up, not fancying the idea of trouble shooting a defective project with 1000 volts floating around. Apart from the question of high voltage

there would seem to be a moral there.

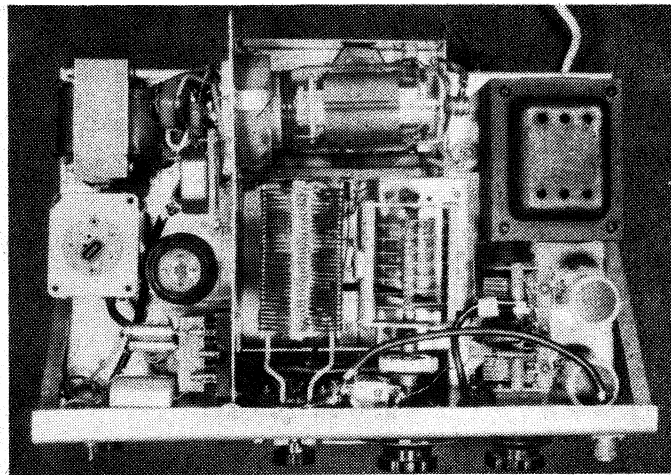Finally a caveat. Despite the fact that the afore described modified rig is regularly heard on 3.62MHz and seems to put out an entirely acceptable signal, the author is an amateur and not an electronics engineer. The project was thus largely assembled and made to work on a cut and try, suck it and see basis. For this purpose a lot of meters, evident in



Internal view of the completed linear amplifier. The 813 output tube is situated at top.

the final equipment, and an oscilloscope have been essential.

The author cannot guarantee that the modifications will work for anyone else or take any responsibility for anyone who misjudges the lethal potential of 1,000 volts at 150 milliamps. With that comment the author will look forward to meeting any other amateur who runs the Tucker Tin, modified or otherwise.